

EE5260: HARDWARE DESCRIPTION LANGUAGE

Take Home Assignment 02

NAME : MUNSIF M.F.A

REG No. : EG/ 2021/ 4684

SEMESTER: 05

DATE : 22 /10 /2024

Task 01:

1.

```
module IC7490 (  
    input wire clk,      // Clock input  
    input wire reset,    // Reset input  
    output reg [3:0] Q // BCD output (QD, QC, QB, QA)  
);  
  
    // Always block for counting functionality  
    always @(posedge clk or posedge reset) begin  
        if (reset) begin  
            Q <= 4'b0000; // Reset to 0  
        end else begin  
            if (Q == 4'b1001) begin  
                Q <= 4'b0000; // Roll back to 0 after reaching 9  
            end else begin  
                Q <= Q + 1; // Increment the count  
            end  
        end  
    end  
end  
  
endmodule
```

2.

```
module IC7490TB;  
    reg clk;  
    reg reset;  
    wire [3:0] Q;  
  
    IC7490 uut (  
        .clk(clk),  
        .reset(reset),  
        .Q(Q)  
    );  
  
    initial begin  
        $dumpfile("counter.vcd");  
        $dumpvars(0, IC7490TB);  
        clk = 0;  
        forever #5 clk = ~clk; // Toggle every 5ns  
    end  
  
    initial begin  
        // Monitor output  
        $monitor("Time = %0t | Reset = %b | Count = %b", $time, reset, Q);  
  
        reset = 1;  
    end  
endmodule
```

```
#10 reset = 0;

#100;

#10 reset = 1;
#10 reset = 0;

#100;

$finish;
end

endmodule
```

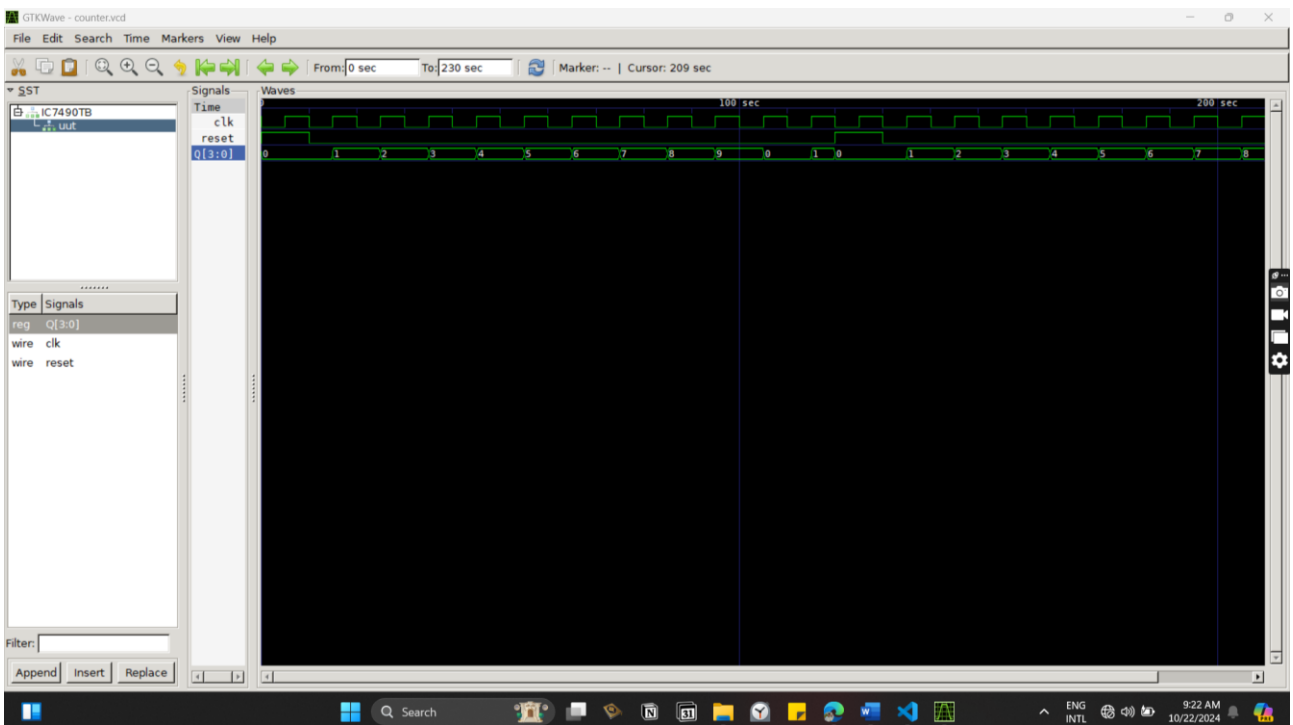


Figure 1: IC7490TB output which displays the BCD Count Sequence

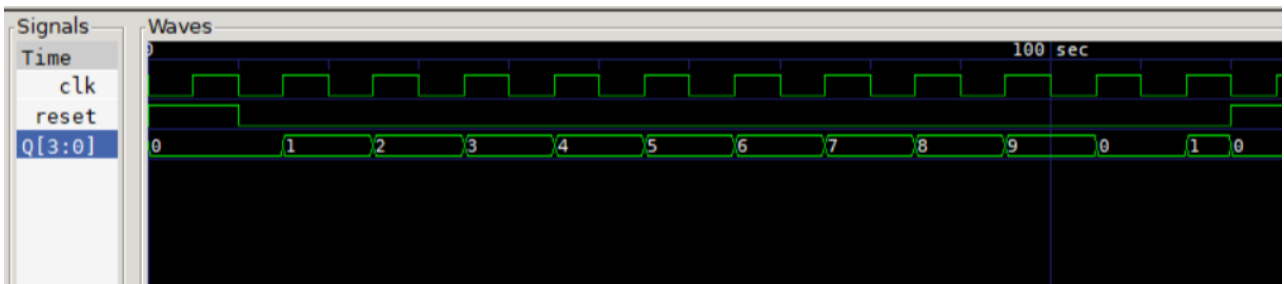


Figure 2: IC7490TB output - zoomed view

Task02:

1.

```
module Decoder (
    input wire [3:0] BCD, // 4-bit BCD input
    output reg [6:0] seg // 7-segment output (a to g)
);
    always @(BCD) begin
        case (BCD)
            4'b0000: seg = 7'b0111111; // 0
            4'b0001: seg = 7'b0000110; // 1
            4'b0010: seg = 7'b1011011; // 2
            4'b0011: seg = 7'b1001111; // 3
            4'b0100: seg = 7'b1100110; // 4
            4'b0101: seg = 7'b1101101; // 5
            4'b0110: seg = 7'b1111101; // 6
            4'b0111: seg = 7'b0000111; // 7
            4'b1000: seg = 7'b1111111; // 8
            4'b1001: seg = 7'b1101111; // 9
            default: seg = 7'b0000000; // For Error Values
        endcase
    end
endmodule
```

2.

```
module IC4017 (
    input wire clk, // Clock input
    input wire reset, // Reset input
    output reg [9:0] Q // 10 output lines (one per count)
);
    reg [3:0] count; // 4-bit counter to track the count (0-9)
    always @(posedge clk or posedge reset) begin
        if (reset) begin
            count <= 4'b0000; // Reset count to 0
            Q <= 10'b0000000001; // Set the first output HIGH
        end else begin
            if (count == 4'b1001) begin
                count <= 4'b0000; // Reset count after 9
            end else begin
                count <= count + 1; // Increment the count
            end
            // Shift the output Q to reflect the current count
            Q <= (10'b1 << count); // Set only one bit HIGH at a time
        end
    end
endmodule
```

Task03:

1.

```
module Counter (
    input wire clk,          // Clock input
    input wire reset,        // Reset input
    output wire [6:0] seg_tens, // 7-segment display for tens
    output wire [6:0] seg_ones  // 7-segment display for ones
);

    reg [5:0] count; // 6-bit counter to count up to 40
    wire [3:0] tens, ones; // BCD digits for tens and ones

    // Increment the counter on each clock pulse
    always @(posedge clk or posedge reset) begin
        if (reset) begin
            count <= 6'b0; // Reset the counter to 0
        end else if (count == 6'd40) begin
            count <= 6'b0; // Reset the counter when it reaches P (40)
        end else begin
            count <= count + 1; // Increment the counter
        end
    end

    // Convert the count into BCD digits for tens and ones
    assign tens = count / 10; // Tens digit
    assign ones = count % 10; // Ones digit

    // Use the Decoder module to drive the 7-segment displays
    Decoder decode_tens(.BCD(tens), .seg(seg_tens));
    Decoder decode_ones(.BCD(ones), .seg(seg_ones));

endmodule
```

2.

```
module CounterTB();

    reg clk;          // Testbench clock
    reg reset;        // Testbench reset
    wire [6:0] seg_tens; // Tens 7-segment output
    wire [6:0] seg_ones; // Ones 7-segment output

    // Instantiate the Counter module
    Counter counter_inst (
        .clk(clk),
        .reset(reset),
        .seg_tens(seg_tens),
```

```

        .seg_ones(seg_ones)
    );

    // Clock generation

    initial begin
        clk = 0;
        forever #5 clk = ~clk; // Toggle the clock every 5 time units
        $dumpfile("counter_wave.vcd");
        $dumpvars(0, CounterTB);
    end

    // Simulation procedure
    initial begin
        reset = 1;    // Start with reset active
        #10 reset = 0; // Deactivate reset after 10 time units

        // Let the counter run for a few clock cycles until it counts to 40
        #415;

        $finish;    // End the simulation
    end

    // Monitoring the output
    initial begin
        $monitor("Time = %0t, Tens = %b, Ones = %b", $time, seg_tens, seg_ones);
    end

endmodule

```

 


Figure 3: CounterTB module's output count from 0 to 17

 


Figure 4: CounterTB module's output - zoomed view

 


Figure 5: CounterTB module's output until 40 as my final digit of the index number is 4

 


Figure 6: CounterTB module's output up to 40 - zoomed view